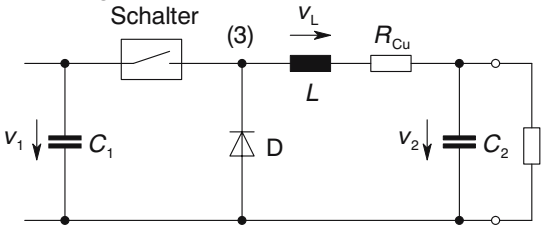


gesteuerter
Schalter



v_1 ↓
 C_1

(3)
 v_L →
 L

R_{Cu}

v_2 ↓
 C_2